

Verification of First Distributive law of Boolean Algebra

Beere Suresh

Abstract—This document shows the verification of first distributive law of Boolean Algebra through Truth Table

Arduino	2	3	4	5	5V	GND								
7447	A	B	C	D	VCC	GND	a	b	c	d	e	f	g	
Sevenseg					COM		a	b	c	d	e	f	g	

TABLE III
2.1 CONNECTIONS

I. STATEMENT

This law states that $X.(Y+Z) = X.Y + X.Z$

This law can be verified by the Truth table mentioned below:

X	Y	Z	Y+Z	X.(Y+Z)	X.Y	X.Z	X.Y + X.Z
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

TABLE I
1.1 TRUTH TABLE

II. COMPONENTS

Component	Value	Qunatity
Resistor	220Ohm	1
Decoder	7447	1
Arduino	UNO	1
Jumper Wires	M-M	20
BreadBoard		1
Sevenseg Display		1

TABLE II
1.1 COMPONENTS

III. HARDWARE

Problem 2.1. Connect COM of Seven Segment Display to the 5V with a resistor of 220 Ohms in series.

Problem 2.2. Make connections between the Arduino UNO, 7447 and Sevenseg Display as shown in Table 2.1

IV. SOFTWARE

Problem 3.1 Now execute the following program and verify the outputs as mentioned in Table 3.1 by modifying the inputs X, Y, Z.

```
wget https://github.com/sureshoye/IDE-Assignment/blob/main/distributivelaw.cpp
```

TABLE IV

Note: You will obtain the result as 0 in the sev-segment display for the given code.